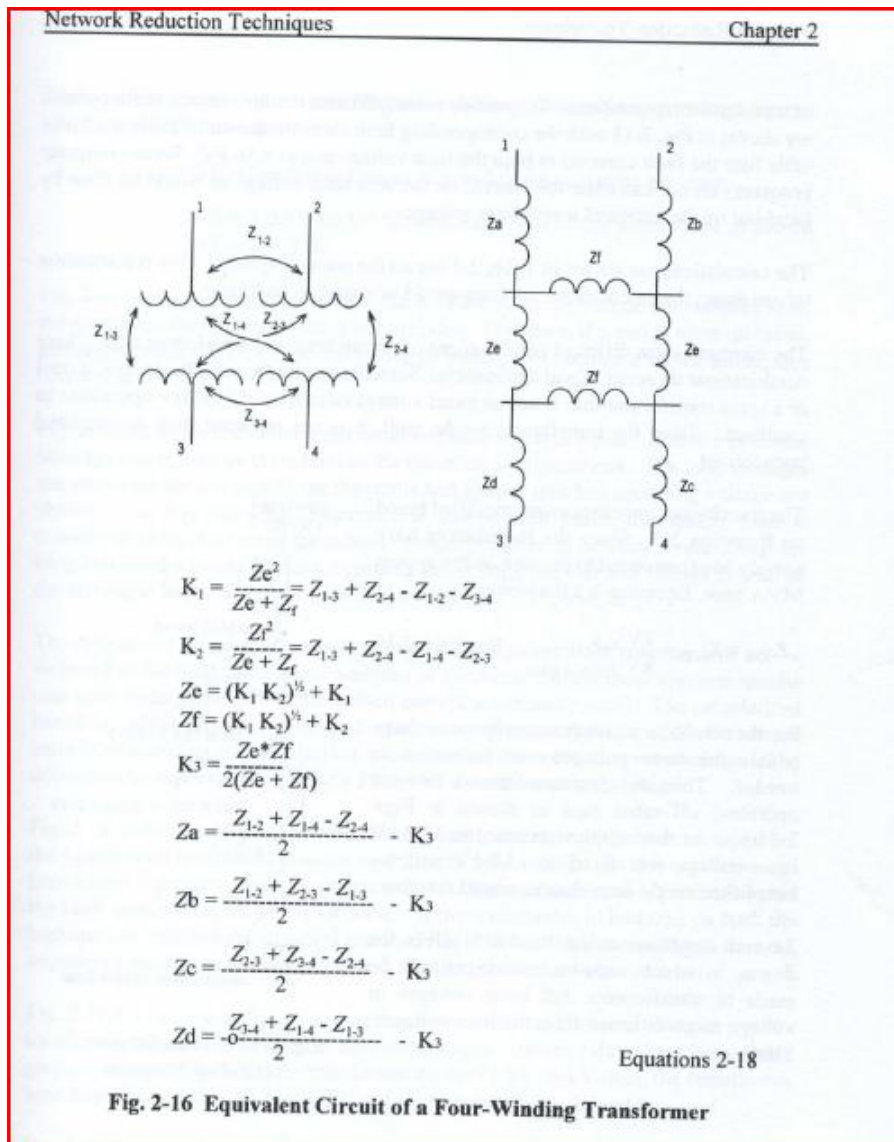


How do I model Four Winding Transformer in PTW?

Solution:

Using as reference "A Practical Guide to Short-Circuit Calculation" by Conrad St. Pierre, Page 37, users can model four-winding transformer as an 8 buses system.



Technical Support Group

Originated by: Mr.Li/Lowell

Date: 03/24/09

Checked by: Mr.Li/Lowell

Date: 03/24/09

Revised by:

Date: 03/24/09

Applicable to: All Version

Doc Rev No: 0



P.O. Box 3376, Manhattan Beach, CA 90266 - Tel: 310.698.4700, Fax: 310.698.4708 - www.skm.com

Four winding Transformer model can be modeled as an 8-bus system.

Example 1

To make things simple, assume $Z_{13}=Z_{24}=Z_{12}=Z_{34}=Z_{14}=Z_{23}=6.5\%$. This means that the transformer is closely coupled/made. So that $K_1=K_2=Z_e=Z_f=0$.

This model can be translated into:

```
K1= Z13+Z24-Z12-Z34;  
K2= Z13+Z24-Z14-Z23;  
Ze = sqrt(K1*K2) + K1;  
Zf = sqrt(K1*K2) + K2;  
if(abs(Ze+Zf) < 0.00001)  
  K3 = 0.;  
else  
  K3=Ze*Zf/2./(Ze+Zf);  
Za=(Z12+Z14-Z24)/2. -K3;  
Zb=(Z12+Z23-Z13)/2. -K3;  
Zc=(Z23+Z34-Z24)/2. -K3;  
Zd=(Z34+Z14-Z13)/2. -K3;
```

Given:

$Z_{13}=Z_{24}=Z_{12}=Z_{34}=6.5\%$

Results:

$K_1=K_2=Z_e=Z_f=0$.

$Z_a=Z_b=Z_c=Z_d= 3.25\%$

Technical Support Group

Originated by: Mr.Li/Lowell

Date: 03/24/09

Checked by: Mr.Li/Lowell

Date: 03/24/09

Revised by:

Date: 03/24/09

Applicable to: All Version

Doc Rev No: 0




Below are results of example1 using an Excel calculator:
Example 1:

Z12	Z13	Z14	Z23	Z24	Z34
6.5	6.5	6.5	6.5	6.5	6.5

K1=	0
K2=	0
Ze=	0
Zf=	0
K3=	0
Za=	3.25
Zb=	3.25
Zc=	3.25
Zd=	3.25

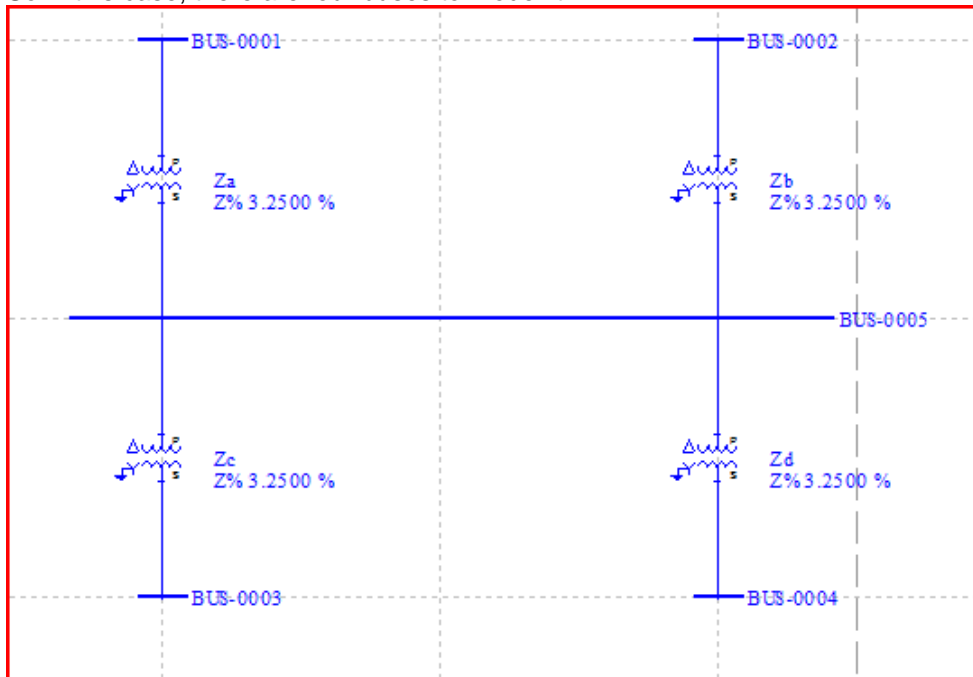So in this case, there are four buses to model it.



Technical Support Group

Originated by: Mr.Li/Lowell

Date: 03/24/09

Checked by: Mr.Li/Lowell

Date: 03/24/09

Revised by:

Date: 03/24/09

Applicable to: All Version

Doc Rev No: 0




Example 2

Given: $Z_{13}=5.5\%$, $Z_{24}=5.5\%$, $Z_{12}=6.5\%$, $Z_{34}=5.5\%$

Z12	Z13	Z14	Z23	Z24	Z34
6.5	5.5	5.5	5.5	5.5	5.5

K1=	-1
K2=	0
Ze=	0
Zf=	0
K3=	0
Za=	3.25
Zb=	3.25
Zc=	2.75
Zd=	2.75

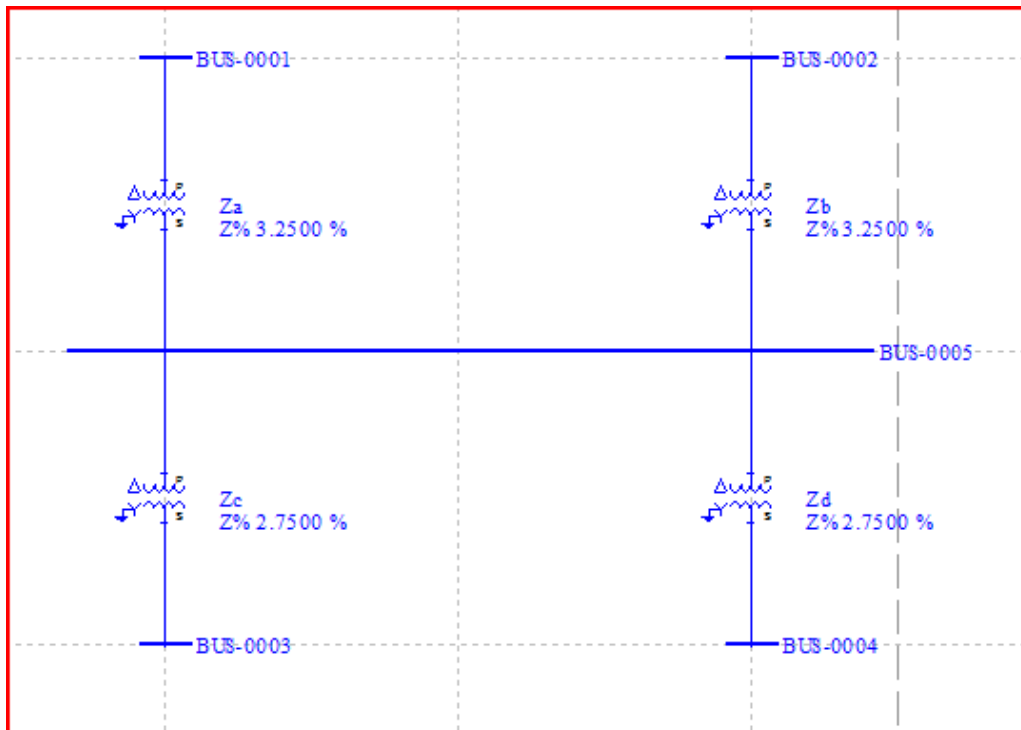

If Z_{13} , Z_{24} , Z_{12} , Z_{34} are not equal, "BUS-0005" could be expanded into 4 buses. (Case 2 is a special case.)
 Z_e and Z_f can be calculated using equations given.

Technical Support Group

Originated by: Mr.Li/Lowell

Date: 03/24/09

Checked by: Mr.Li/Lowell

Date: 03/24/09

Revised by:

Date: 03/24/09

Applicable to: All Version

Doc Rev No: 0



P.O. Box 3376, Manhattan Beach, CA 90266 - Tel: 310.698.4700, Fax: 310.698.4708 - www.skm.com